



Daffodil International University  
Department of Electrical and Electronic Engineering  
Faculty of Engineering  
**Final Examination, Fall – 2024**

Course Code: 0713-121  
Section: A, B, C  
Full Marks: 40


Course Title: Electrical Circuits II  
Level-Term: L1-T2  
Exam Date: December 18, 2024

Teacher's Initial: MSA, SZE  
Time: 2 Hours

*Taking at least TWO from each section, answer FIVE of the following questions.*


**Section A**

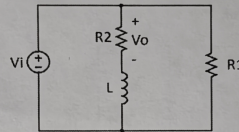- Q1. (a)** Determine the type of filter the following circuit works as. Find the corner frequency if  $R_1 = 200\Omega$ ,  $R_2 = 100\Omega$  and  $L = 2\text{mH}$ . CO-3 [04]  
(C5)



- (b)** A band Stop Filter circuit's rejection frequency is 1000 Hz, and the rejection bandwidth is 500 Hz. if  $L = 0.1\text{H}$ , **design** the circuit with suitable values of R and C. (C6) [04]

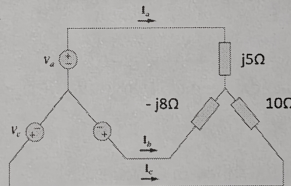- Q2. (a)** Compute the phase currents of the following 3-phase unbalanced circuit operating in abc sequence if  $V_{an} = 120\text{ V}$ . CO-2 [06]  
(C3)



- (b)** Calculate the total complex power of the load. [02]

- Q3. (a)** Show that for a three-phase balanced load,  $Z_{\Delta} = 3Z_Y$ . CO-2 [02]  
(C3)

- (b)** For a 3-phase Y-connected source, **prove** that  $V_L = \sqrt{3}V_P \angle 30^\circ$ . [02]

- (c)** In a 3-phase negative sequence balanced Y- $\Delta$  circuit,  $V_{an} = 100 \angle 0^\circ$  and the per phase impedance,  $Z_{\Delta} = (12 - j6)\Omega$ . **Compute** the line voltages, line currents, total power, and power factor of the system. [04]


- Q4. (a)** **Demonstrate** the expression of resonant frequency ( $\omega_0$ ) in an R-L-C series resonant circuit. **Sketch** the frequency response of the circuit with proper labelling. CO-3 [03]  
(C3)

- (b)** A three-phase  $\Delta$ -connected motor takes 20KVA power with 0.6 power factor (lagging). The motor is connected to a Y load of  $15\Omega$  resistance and  $12\Omega$  inductive reactance connected in series in each phase. **Calculate** the total Volt-Amperes, power factor, and line current of the circuit. CO-2 [05]  
(C3)


**Section B**

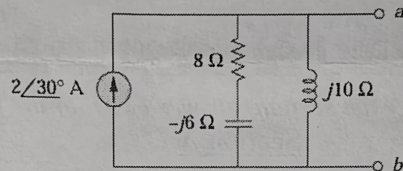**Q5. (a)** Show that in a Thevenin's equivalent circuit, maximum power is attained if the load impedance,  $Z_L = Z_{th}^*$  where,  $Z_{th}$  = Thevenin's equivalent impedance. CO-2 [04]  
(C3)


**(b)** Compute the Thevenin's equivalent of the circuit. What is the maximum power of the load? [04]



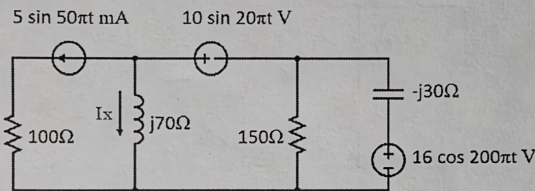**Q6. (a)** Write the expression of  $I_x$  of the following circuit. CO-2 [05]  
(C3)




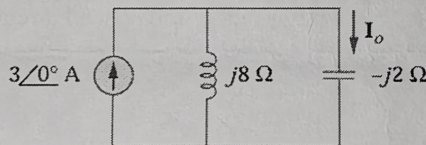**(b)** Determine  $I_o$  of the following circuit using Mesh analysis. (C5) [03]



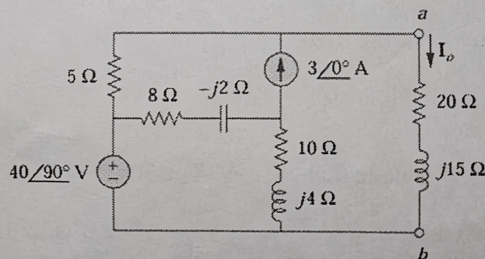**Q7. (a)** What do you understand by a sinusoidal signal? Prove that a signal's RMS value is always greater than the AVERAGE value. CO-2 [03]  
(C1)

**(b)** Calculate the Norton's equivalent of the following circuit. (C3) [05]



**Q8. (a)** Use nodal analysis to find  $I_x$  of the following circuit. CO-2 [08]  
(C3)

