

Daffodil International University Department of Software Engineering Faculty of Science & Information Technology

Midterm Examination, Fall 2023

Course Code: SE 213; Course Title: Digital Electronics & Logic design

Batch: 40 & 38; Sections: All

Time: 1:30 Hrs

Marks: 25

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

1	Ý	Develop the truth table and circuit diagram of the following Function $F = xy(y'+z) + x'z'$	[Marks-4]	CLO-1 Level-3
3	bS	Utilize 2's complement method to Subtract the binary numbers 101101 - 110011	Marks-3	
2	<u>E</u>	Explain why the NOR gate is referred to as a universal gate.	[Marks-3]	
2	gy	Y=BC+AC'+AB+BCD Apply k-map simplification technique to simplify the above expressions. Construct the logic diagrams of the simplified output.	[Marks-4+3]	CLO-2 Level-3
	B	Check the following function. Interpret in sum of minterms & convert it to product of maxterms form.	Marks-8	
		F(W,X,Y,Z)=Z(W'+X)+X'Z Kawsher HRidoy		