



Daffodil International University
Faculty of Science & Information Technology
Department of Computer Science and Engineering

Final Examination, Spring-2024

Course Code: CSE121 Course Title: Electrical Circuits
 Level: 1 Term: 2 Batch: 65


Time: 2 Hours

Full Marks: 40

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

| | | | |
|-----|--|--------|-----|
| Q1. | a) Explain the concept of super node. b) Illustrate the periodic waveform of sinusoidal voltage with peak amplitude and peak-to-peak value. c) Compare the phasor diagram and impedance diagram for the series circuit. d) Interpret the power factor of inductive network. e) Show the complex conjugate of a complex number in rectangular form. | 5x2=10 | CO1 |
| Q2. | a) Solve the equivalent resistance and the value of the current through 10.4 kΩ of the following circuit. <div style="text-align: center; margin-top: 20px;"> </div> | 6x2=12 | CO2 |

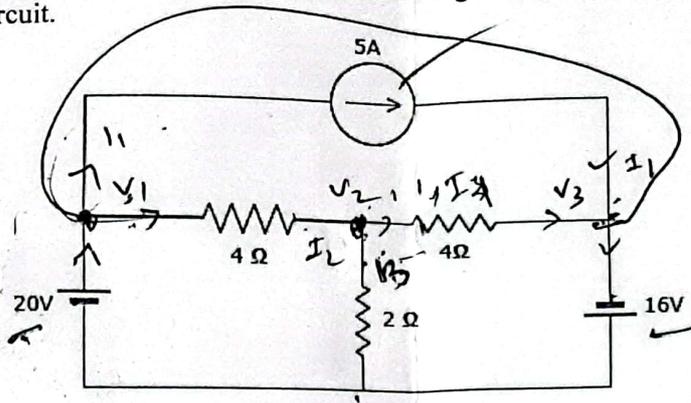b) Apply nodal analysis to determine the voltage across 2Ω resistance in the following circuit.



Q3. a) Simplify the following equation to determine the effective values of the waveforms followed by I-V plot and also the average power loss of the circuit whose input current and voltage are as follows:

6x3=18 CO3

- i. $i = 7\sin(377t - 70^\circ)$
- ii. $v = 263.9\sin(377t + 20^\circ)$

b) The current through a 0.2 H coil is provided.

$$i = 8.5\sin(377t - 55^\circ)$$

Now Simplify the following equation to find:

- i. The sinusoidal expression for the voltage.
- ii. Sketch the v and i curves.
- iii. Power factor of the v and i and indicate they are leading or lagging.

c) Examine the following R-L circuit to determine the Z_T , I , V_R , V_L , P_T followed by phasor diagram:

