

SOLVED



Daffodil International University

Faculty of Science & Information Technology

Department of Computer Science and Engineering

Final Examination, Summer - 2026

Course Code: CSE215 Course Title: Electronic Devices and Circuits

Level: 2 Term: 2 Batch: 68

Marks: 40

Exam Duration: 2 Hours

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

1.	a)	Draw the block diagram of multistage amplifier.	[2]	CO1
	b)	Define feedback and state its significance in electronic amplifiers.	[2]	
	c)	Define faithful amplification and state the conditions required to achieve it.	[2]	
	d)	State the role of Emitter bypass capacitor (C_E) and Coupling capacitor (C_C).	[2]	
	e)	List the Ideal characteristics of OP-Amp.	[2]	
2.	a)	Describe the working principle of E-MOSFET with necessary diagram.	[5]	CO2
	b)	Discuss tank circuit with necessary circuit diagram.	[5]	
3.	a)	A 1 pF capacitor is available. Calculate the inductor values in a Hartley oscillator so that $f = 1 \text{ MHz}$ and $m_v = 0.2$.	[5]	CO3
	b)	In a transistor circuit shown in Fig. 01, determine the operating point. Assume silicon transistor is used.	[5]	

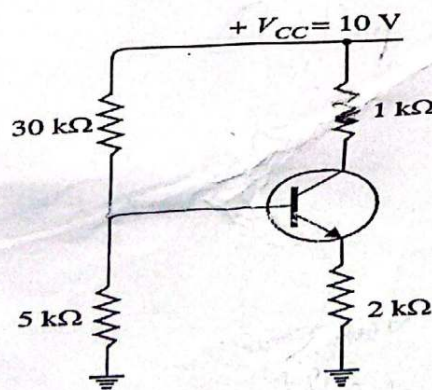


Fig. 01

c)	An amplifier has an open-loop gain $A_v = 100,000$. Negative feedback of 10 db is applied. Solve for: (i) voltage gain with feedback (ii) value of feedback fraction m_v .	[5]	
d)	Determine the value of I_C for voltage divider method if $V_{CC} = 9V$, $R_E = 1k\Omega$, $R_1 = 39 k\Omega$, $R_2 = 10 k\Omega$, $R_C = 2.7 k\Omega$, $V_{BE} = 0.15 V$ and $\beta = 90$.	[5]	

ANSWER SHEET (Mathematical Questions Only)

Q3(a) Hartley Oscillator - Inductor values ($C = 1 \text{ pF}$, $f = 1 \text{ MHz}$, $m_v = 0.2$):

$$L1 = 4.22 \text{ mH}$$

$$L2 = 21.11 \text{ mH}$$

$$(L1 + L2 = 25.33 \text{ mH})$$

Q3(b) Operating Point of Transistor Circuit (Fig. 01):

$$V_B = 1.43 \text{ V}$$

$$V_E = 0.73 \text{ V}$$

$$I_E = I_C = 0.364 \text{ mA}$$

$$V_{CE} = 8.91 \text{ V}$$

Q3(c) Amplifier with Negative Feedback ($A_v = 100,000$, $FB = 10 \text{ dB}$):

$$(i) A_{vf} = 31,623$$

$$(ii) m_v = 2.16 \times 10^{-5}$$

Q3(d) IC using Voltage Divider Method:

$$V_{TH} = 1.84 \text{ V}$$

$$R_{TH} = 7.96 \text{ k-ohm}$$

$$I_B = 17.05 \text{ uA}$$

$$I_C = 1.53 \text{ mA}$$