



Daffodil International University

Department of Computer Science and Engineering

Faculty of Science & Information Technology

Midterm Examination, Fall 2022


Course Code: 223, Course Title: Digital Electronics

Level: 2 Term: 2 Batch: 59

Time: 02:00 Hrs

Marks: 40

Answer ALL Questions

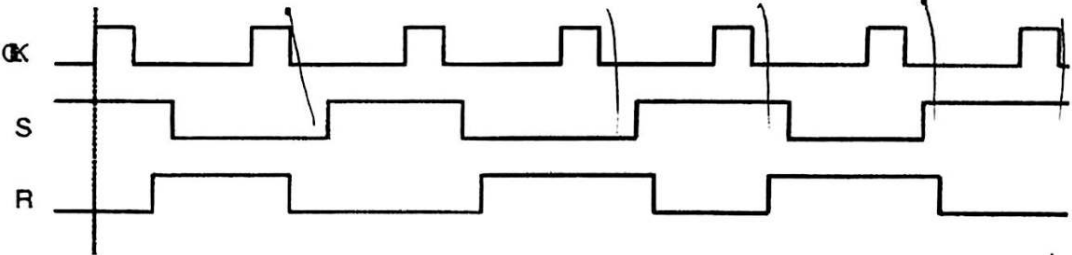1.	a)	A global electrical juncture is now occurring. We must save power in order to get out from this circumstances. You need to develop a system to <u>diminish</u> the amount of power used in your home. Imagine that you had a <u>television</u> , <u>fan</u> , <u>air conditioner</u> , and <u>light</u> in your home, but you can only use <u>two</u> of these at once. Now develop truth table, Boolean expression and circuit for the system.	[10]	CO2
2.	a)	Construct 4 to 16 line decoder with four 2 to 4 line decoder.	[5]	CO3
	b)	Construct 4 to 2 line Priority Encoder where I_3 holds top priority.	[5]	
	c)	Implement the following Boolean function with a multiplexer. $F(A, B, C, D) = \sum (0, 2, 4, 5, 8, 10, 11, 14)$	[5]	
	a)	Compare sequential circuit and combinational circuit.	[5]	CO4
	b)	Determine the output states Q and Q' for S-R flip flop, given the following pulse inputs. 	[10]	