



Daffodil International University
Department of Electrical and Electronic Engineering
Faculty of Engineering

Final Term Examination, Spring 2026

Course Code: **0713-213**
Section: A, B, C, D
Full Marks: **40**

Course Title: **Energy Conversion I**
Level-Term: **1-2 - T1**
Exam Date: **April 25, 2026**

Teacher's Initial: **DRA, PA**
Time: **2.0 Hours**

Attempt to Answer all of the 4 Questions

The second right most column indicates the course outcomes with respective Bloom's level and right most column indicates the allocated marks

Q1. a) Explain in your own words **any two** of the following:

Auto-Transformer, Single-Phase Induction Motor, Induction Generator, Parallel Operation of Transformers.

[4]

Q1. b) A 4-pole, 50-Hz, 3- Φ induction motor develops a maximum torque of 60.8 Nm at 1375 rpm. The resistance of the star-connected rotor is 0.15 Ω /phase. **Calculate** the value of the resistance that must be inserted in series with each rotor phase to produce a starting torque equal to $3/4^{\text{th}}$ of the maximum torque.

[4]

Q2. a) Show that a transformer achieves maximum efficiency when copper losses are equal to iron losses. CO-2 [3]
C(2)

Q2. b) A 5.6 kVA, 50 Hz, 250/400 V single-phase transformer undergoes open-circuit and short-circuit tests with the following test data:
Open-circuit test: Voltage = 250 V, Current = .5 A, Power = 80 W – on LV side
Short-circuit test: Voltage = 20 V, Current = 20 A, Power = 50 W – HV shorted
Calculate (i) equivalent circuit parameters w. r. to LV side, (ii) efficiency and (iii) the terminal voltage on the HV side when it supplies $1/4^{\text{th}}$ of full load with a 0.8 power factor lagging, the supply voltage being 250 V. CO-2 [6]
C(4)

Q3. a) Prove that maximum starting torque is achieved when rotor resistance is equal to rotor reactance. CO-2 [3]
C(2)

Q3. b) 3-phase induction motor having a 6-pole, star-connected stator winding runs on 250 V, 50-Hz supply. The rotor resistance and standstill reactance are 0.12 ohm and 0.85 ohm per phase. The ratio of stator to rotor turns is 1.8. Full load slip is 4%. Calculate the developed torque at full load, maximum torque and speed at maximum torque. CO-2 [6]
C(4)

P.T.O.

Page 1 of 2

250

$$P = VI$$

$$\Rightarrow I = \frac{P}{V} \times \frac{1}{4}$$

$$= \frac{50}{100} \times \frac{1}{4}$$

$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_{in} = \frac{P_{out}}{\eta}$$

Answer any 2 (Two) from the following 3 (Three) questions:

Q4. a) A 230-V, 3- ϕ , 4-pole, 50-Hz, Y-connected induction motor is rated 3.8 kW. The equivalent circuit parameters are: $R_1 = 0.4 \Omega$, $X_1 = 0.8 \Omega$; $R_2' = 0.45 \Omega$, $X_2' = 1.2 \Omega$, $X_m = 30 \Omega$. The stator core loss is 60 W and rotational loss is 140 W. For a slip of 0.04, compute: (i) input current, I_1 (ii) air-gap power, P_g (iii) mechanical power, P_m (iv) gross torque, T_g (v) output power, P_{out} and (vi) efficiency, η . CO-3 [7] C(5)

Q4. b) A 120V, 60-Hz, 3-phase, Y-Connected, 6-pole induction motor has an equivalent T-circuit consisting of stator impedance of $0.07 + j 0.3 \Omega$ and an equivalent rotor impedance at standstill of $(0.08 + j 0.3) \Omega$. Magnetizing branch has $X_m = 6.33 \Omega$, $R_0 = 45.45 \Omega$. Determine (a) rotor current, I_2' (b) stator current, I_1 (c) primary p.f. (d) gross power output, P_g (e) gross torque, T_g (f) input power, P_1 and (g) gross efficiency by using approximate equivalent circuit. Assume a slip of 2%. CO-3 [7] C(5)

Q4. c) A 10-kVA distribution transformer has a full-load efficiency at unity p.f. of 98%, the copper and iron losses then being equal. Calculate its all-day efficiency if it is loaded throughout the 24 hours as follows: One-fourth load for 10 hours; Quarter load for 3 hours; Half load for 6 hours; and Full load for 5 hours. Assume load p.f. of unity. CO-3 [7] C(5)