



Daffodil International University

Faculty of Science & Information Technology

Department of Computer Science & Engineering

Final Examination, Fall 2025

Course Code: CSE223, Course Title: Digital Logic Design


Level: 2 Term: 2 Batch: 66

Time: 02:00 Hrs

Marks: 40

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

 1.	a) An automated campus parking gate uses three binary sensors and one control signal: • E: Entry sensor (1 = vehicle entering detected, 0 = none) • X: Exit sensor (1 = vehicle exiting detected, 0 = none) • R: Reserve/override button (1 = Reserve mode active, 0 = normal) • CLK: System clock (edge triggered) Design a 3-bit bidirectional car occupancy counter (counts current cars in lot) with range 0 to 7 and the following control logic: 1. When E = 1 and R = 0, the counter increments by 1 on the next clock (vehicle entered). 2. When X = 1, the counter decrements by 1 on the next clock (vehicle exited). If both E and X = 1 simultaneously, they cancel and the count does not change. 3. If the count reaches 7 (full), a FULL LED should be ON; further entry attempts (E=1) while at 7 must not increase the count. 4. If the count is 0 (empty), an EMPTY LED should be ON; further exit attempts (X=1) while at 0 must not decrease the count. 5. When R = 1 (Reserve mode), no new entries are permitted — E must be ignored for incrementing; exits still decrement the count. Tasks: a) Build the complete truth table / state-action table covering inputs (E, X, R) and present state (Q2 Q1 Q0) to next state (Q2+ Q1+ Q0+) and outputs (FULL, EMPTY). b) Choose a flip-flop type (D or JK or T) and derive the flip-flop input equations required to implement the next-state logic. c) Draw the logic circuit diagram (flip-flops + combinational logic) implementing the counter and FULL / EMPTY indicators. Indicate clocking and any necessary gating for the Reserve input.	10	CO3
	b) $F(A,B,C,D) = \sum(0, 1, 4, 5, 9, 10, 14, 15)$ Implement the following function using multiplexer, where C, D is input and A, B selector.	5	
2.	a) For the positive edge triggered Flip-Flop determine the following output timing diagram Q and Q' with the given state of S, R, and CLK in figure below. The flip-flop is initially in SET state. Now draw the timing diagram of Q and Q'. 	5	CO4

	b)	State the difference between latch and flip-flop.	5	
3.	a)	A communication system stores data in a 4-bit word 1110, where all four bits are loaded into the flip-flops simultaneously but need to be transmitted one bit at a time to another device. Based on this requirement, apply your understanding to identify the type of register suitable for this operation explaining the process. Design block diagram and truth table to illustrate how the bits move through the circuit.	5	
	b)	Draw a block diagram 4-bit binary synchronous up counter.	5	
	c)	Implement the following Boolean expression using PAL, $F1 = \sum m(3,5,7)$ and $F2 = \sum m(4,5,7)$	5	

Note: You may add or delete rows as per your requirements. Mention CO's in the right side of the table as per your course outline.