

Daffodil International University  
Faculty of Science & Information Technology  
Department of Software Engineering  
Midterm Examination, Summer 2026

**Course Code: SE 213; Course Title: Digital Electronics & Logic design**  
Sections & Teachers: A-D(SP), E-H(NIR), I(DAT), J-L(SIK), M(KRY), N(MTE), O(KNA), P(FT)

**Time: 1 Hour 30 Mins**

**Marks: 25**

**Answer ALL Questions**

*[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]*

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  |           |                  |
|----|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------|------------------|
| 1. | <p>a) Compute the following arithmetic operation:</p> $(9AF.8A)_{16} + (476.466)_8 = (?)_{10}$ <p>b) Show the binary arithmetic operation Division, where Dividend is 1001011 and Divisor is 101.</p> <p>c) A software engineer is debugging a low-level embedded system where memory addresses are represented using 8-bit binary numbers. During execution, the program calculates the offset between two memory locations stored in separate registers. The two registers R<sub>1</sub> and R<sub>2</sub> have the following values stored:</p> $R_1 = (00110101)_2$ $R_2 = (00001111)_2$ <p>To determine the relative displacement, the processor performs subtraction using the 2's complement arithmetic method, rather than direct binary subtraction. The final value is stored in the Result Register (RR).</p> <p>Calculate the value that will be stored in the Result Register (RR) after execution of the following operation:</p> $RR = R_1 - R_2$ <p>Use the 2's complement technique to perform the subtraction and express the final result in binary form.</p> | [Marks-4] | CLO-1<br>Level-2 |
| 2. | <p>a) The Daffodil International University Library is a large single-floor facility. It uses a smart digital lighting system to control the lights automatically. You have been assigned to design a logic-based monitoring system to determine whether the Library Light (L) should be turned ON.</p> <p>Inputs (Sensors):</p> <ul style="list-style-type: none"> <li>D: Dark Level (D = 1 if it is dark outside, D = 0 if there is daylight)</li> <li>C: Close Status (C = 1 if the library is supposed to be closed, C = 0 if it is open)</li> </ul>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                         | [Marks-4] | CLO-2<br>Level-3 |

|    |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                         |           |
|----|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----------|
|    | <ul style="list-style-type: none"> <li>P: Presence Status (<math>P = 1</math> if people are inside the library, <math>P = 0</math> if the library is empty)</li> </ul> <p>Output:</p> <ul style="list-style-type: none"> <li>L: Library lights (<math>L = 1</math> lights ON, <math>L = 0</math> lights OFF)</li> </ul> <p>Light will follow this condition:</p> <ol style="list-style-type: none"> <li>If the library is open <u>and</u> it is dark outside, regardless of how many people are present.</li> <li>If the library is open, people are present <u>and</u> if it is daylight.</li> </ol> <p>Based on the above rules, <b>derive</b> the Boolean equation for the output L and <b>construct</b> the truth table for all possible input combinations (in the order CDP).</p> |           |
| b) | $F = (J + K) + (\overline{K} + L)$ <p>Simplify the above expression. <b>Construct</b> the logic diagrams of the simplified output.</p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  | [Marks-4] |
| c) | <p><math>F(A, B, C, D) = \sum(0, 2, 6, 7, 8, 10, 14, 15)</math></p> <p>Apply k-map simplification technique to <b>derive</b> the most simplified version of the above expressions.</p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  | [Marks-4] |
| d) | <p><b>Apply</b> Parallel adder to compute <math>(P + Q)</math> along with diagram: Where <math>P = 101101</math> and <math>Q = 11011</math></p>                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                         | [Marks-3] |

1001000