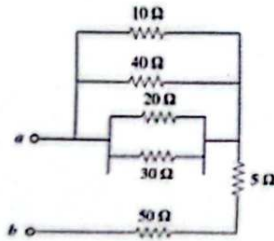


Quiz-1, Course: Electrical Circuit, Course Code: CSE121

Section: 70_M

Find the equivalent resistance at terminals $a-b$



1.

