



Daffodil International University
Department of Electrical and Electronic Engineering, Faculty of Engineering
Final Examination, Summer- 2026

25/28
Ans.

Course Code: 0714- 221

Course Title: Electronics II

Section: A, B, C, D

Level-Term: L2-T2

Teacher's Initial: SR, MH

Full Marks: 40

Date: 27-Aug., 2026

Time: 2.00 Hours

[Notes: Answer all the following questions]

[The second right most column indicates the course outcomes with respective Bloom's level and right most column indicates the allocated marks]

- Q1.** A series-tuned antenna circuit consists of a variable capacitor (60 pF to 380 pF) and a 200- μ H antenna coil that has a dc resistance of 10 Ω . CO-3
C5 04
- Find the frequency range of radio signals to which the radio is tunable.
 - Determine the value of Quality Factor, Q at each end of the frequency range

- Q2.** A biomedical signal acquisition system needs to pass only a specific frequency band of interest and suppress all other frequencies. The design requires a first-order active band-pass filter formed by cascading first-order high-pass and low-pass stages. CO-3
C5 04

Design specifications:

- Lower cutoff frequency: 100 Hz
- Upper cutoff frequency: 1 kHz
- Overall gain: 20
- Select capacitor values: High-pass stage: 0.3 μ F & Low-pass stage: 0.01 μ F

Determine:

- a. Resistor values for both stages
- b. The center frequency and bandwidth
- c. **Design** the final band pass filter circuit for the required specifications.

- Q3.** (i) **Explain** the working principle of 555 timer in astable mode. CO-3
C2 04

- (ii) **Design** a multivibrator with 555 timer in astable mode which produces a square wave of 2 MHz and duty cycle will be 60%. CO-3
C5 04

- Q4.** (i) **Explain**, with mathematics and graphical illustration, how positive feedback enables an oscillator to produce an undamped sinusoidal oscillation without any external input, explain based on the Barkhausen criterion. CO-3
C2 04

- (ii) **Explain** the circuit operation of Colpitt's Oscillator. Focus how feedback circuit can produce a phase shift of 180° and show the frequency of oscillation and feedback fraction. CO-3
C2 04

- (iii) **Design** a Hartley oscillator to produce a sine wave of frequency 96 MHz, use Capacitors of LC tank circuit C=12 pF. And consider the feedback fraction $m_v=0.1$ (Find the parameter values and **Draw** the Complete **Designed Circuit**) CO-3
C4 04

- Q5. Analyze and find the transfer function and pass band gain (as a function corner frequency of low pass and high pass filter) of the below filter circuit given in Fig. 1. What kind of filter is it? CO-3 04
C4

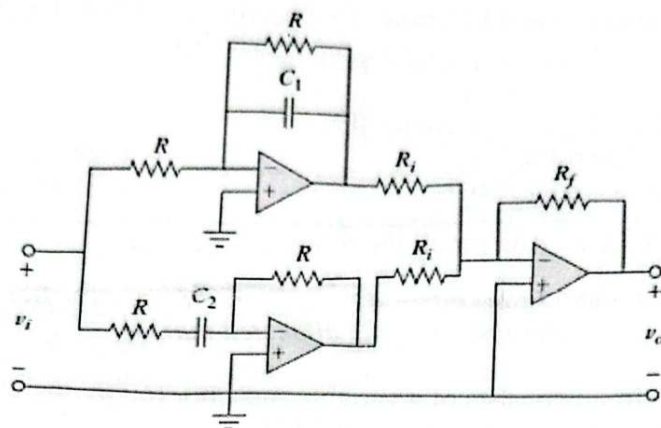


Fig. 1

- (i) Analyze that the Voltage gain with negative feedback of an amplifier is $A_{vf} = \frac{A_v}{1+A_v m_v}$ where the gain of the amplifier without feedback is A_v and feedback fraction is m_v . And Discuss the advantages of Negative Voltage Feedback. CO-2 04
C4
- (ii) An amplifier has a voltage amplification A_v and a fraction m_v of its output is feedback in opposition to the input. If $m_v=0.1$ and $A_v= 300$, calculate the percentage change in the gain of the system if A_v falls 8 db due to ageing. CO-2 04
C3

$$= V_o$$

$$) = V_o$$

$$m_v) = V_o$$

$$A_v m_v = V_o$$

$$V_o + V_o \cdot A_v m_v$$

$$V_o (1 + A_v m_v)$$

$$\frac{V_o}{1 + A_v m_v}$$