



Daffodil International University
Department of Electrical and Electronic Engineering
Faculty of Engineering
Mid-Term Examination, Spring – 2026

Course Code: **0713-213**

Section: A/B/C/D

Full Marks: 25

Course Title: Energy Conversion I

Level-Term: L2-T1

Exam Date: February 22, 2026

Teacher's Initial: DRA / PA

Time: 1.5 Hours

Attempt to Answer all 3 Questions

Q1. a) Draw the phasor diagram of a capacitively loaded transformer with winding resistance and leakage reactance CO-1 [3]
C(3)

b) A 25 kVA, 2500/220 V, 50 Hz transformer has a high-voltage winding resistance of 0.15Ω and a leakage reactance of 0.25Ω . The low-voltage winding has a resistance of 0.04Ω and a leakage reactance of 0.016Ω . Find the equivalent winding resistance, reactance and impedance referred to the (i) high-voltage side and (ii) the low-voltage side and (iii) total Cu loss of the transformer. CO-1 [4]
C(3)

Q2. a) A transformer with magnetic leakage is equivalent to an ideal transformer with inductive coils connected in both primary and secondary side'- Justify this statement with necessary detailing. CO-1 [3]
C(2)

b) A 15 kVA, 450/150 V, 50 Hz transformer is connected to the high-voltage side while the low-voltage side remains open. The transformer draws 0.5 A of current and consumes a power of 25 W. Calculate (i) no-load pf angle and pf, (ii) the magnetizing current, (iii) core loss current. CO-1 [5]
C(3)

Q3. Answer any 2 (Two) from the following questions:

a) The parameters of a 2200/230 V, 50-Hz transformer are given below:
 $R_1 = 0.18 \Omega$; $X_1 = 0.9 \Omega$; $R_2 = 0.45 \Omega$; $X_2 = 0.5 \Omega$; $R_0 = 235 \Omega$; $X_m = 1250 \Omega$. The secondary load impedance $Z = 0.55 + j 0.35 \Omega$. Solve for , , using the exact equivalent circuit with normal voltage applied across the primary. CO-2 [5]
C(4)

b) A 30 kVA, 2200/240 V, 50 Hz transformer has $R_1 = 25 \Omega$, $L_1 = 32 \text{ H}$, $R_2 = 0.05 \Omega$, $X_2 = 1.27 \text{ mH}$, no-load current of 5 A leading the flux by and delivers full-load secondary current of 125 A at 200 V with a power factor of 0.85 lagging. Calculate (i) the supply voltage (ii) the overall power factor and (iii) draw the associated vector diagram. CO-2 [5]
C(4)

c) Obtain the equivalent circuit of a 230/400-V, 50-Hz, single-phase transformer from the following test data :
O.C test : 230 V, 0.8 A, 60 W – on L.V. side
S.C. test : 12 V, 10 A, 115 W – on H.V. side
Calculate the secondary terminal voltage when delivering 5 kW at pf 0.85 lagging, the primary voltage being 230V. CO-2 [5]
C(4)

Nafat