



Daffodil International University
 Department of Electrical and Electronic Engineering
 Faculty of Engineering
Final Examination, Fall 2025

Course Code: 0713-121

Section: A, B, C, D

Full Marks: 40

Course Title: Electrical Circuits II

Level-Term: L1-T2

Exam Date: December 14, 2025

Teacher's Initial: MSA, SZE

Time: 2 Hours

Questions No. 1 and 2 are COMPULSORY. Answer any 3 (THREE) from the rest of the Questions

- Q1.** (a) Distinguish between the frequency response of a BPF and BSF circuit, labeling the graphs properly. CO-3 [04+04
C (4) = 08]
- (b) Explain mathematically what type of filter the circuit in Figure 1(b) works as. Illustrate the actual and ideal frequency response of the corresponding filter.

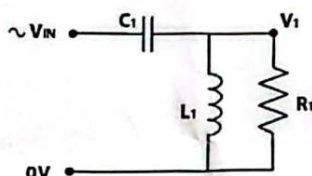


Figure: 1(b)

$$\frac{R \times j\omega L}{R + j\omega L} \rightarrow \frac{1}{R}$$

- Q2.** (a) Deduce the relation of half-power frequencies with circuit elements (R, L, C) of an RLC series resonance circuit. CO-3 [04+04
C (4) = 08]
- (b) The Quality factor of a band-pass filter circuit is 50. If the resonant frequency of the circuit is 5 krad/s , calculate the Bandwidth of the circuit. Also, illustrate the circuit with appropriate values of R and C if $L = 0.1 \text{ H}$.
- Q3.** (a) Show that in a balanced Y-Y circuit, $I_n = 0$. CO-2 [02+02
C (3) +04=08
]
- (b) Illustrate the phasor diagram of the Line and Phase voltages of a Y-connected source.
- (c) Calculate V_x of the circuit in Figure 3(b) using nodal analysis.

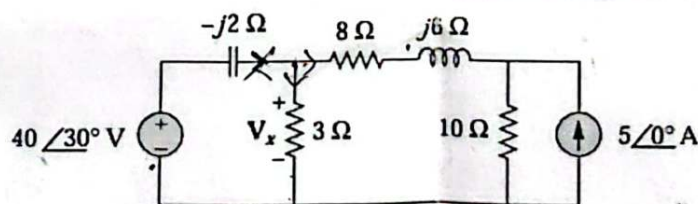


Figure: 3(b)

- Q4.** Calculate the line currents of the load of the 3-phase unbalanced circuit given in Figure 4. **CO-2 [05+03]**
 The circuit is operating in abc sequence $V_{an} = 120\angle 45^\circ$ V. **Show that the total complex power C (3) = 08]**
 supplied by the source equals the total complex power of the load.

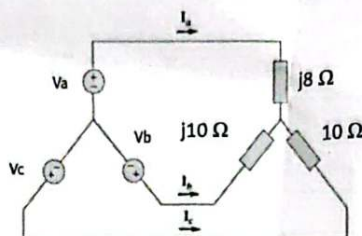


Figure: 4

- Q5.** (a) Explain your understanding of Kirchhoff's Voltage Law (KVL) with a suitable example. **CO-2 [02+06]**
 (b) Compute i_o of the circuit in Figure 5(b). **C (3) = 08]**


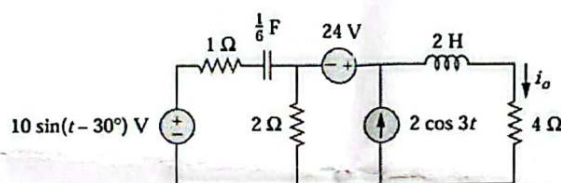


Figure: 5(b)

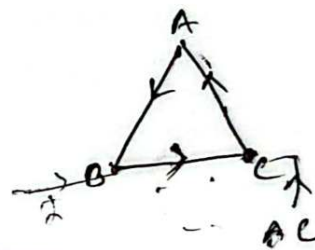

- Q6.** (a) In a balanced Δ -Y circuit, $V_{ab} = 110$ V. The per-phase impedance, $Z_Y = (10 + j5) \Omega$. **CO-2 [04+04]**
 Compute the line voltages, line currents, total power, and power factor of the system if **C (3) = 08]**
 the circuit operates in acb sequence.
 (b) A three-phase wye-connected motor takes 10 kVA at 0.8 power factor lagging from a source of 120V. It is in parallel with a balanced delta load having $12 - j8 \Omega$ impedance per phase. Calculate the equivalent impedance per phase, line currents, and power factor of the combination.
- Q7.** (a) A 5-horsepower, 220V, three-phase motor has an efficiency of 70 percent and operates with a line current of 15 A. **CO-2 [02+06]**
 Compute the power factor at which the motor is operated. **C (3) = 08]**
 (b) Use Mesh Analysis to compute the current I_o flowing in the circuit in Figure 7.

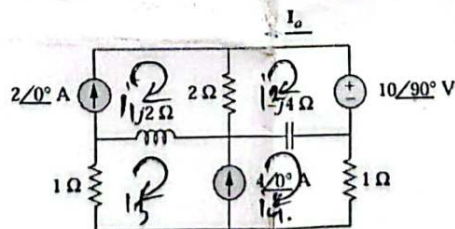


Figure: 7

$$I = \frac{V}{R}$$

$$V = IR$$

$$\Rightarrow R = \frac{V}{I}$$