

Quiz – 01

Electrical Circuits II [0713-121]

Full Marks: 15


Time: 15 Minutes

ID:

Section:

Q1. Calculate I of the following circuit.

(10)

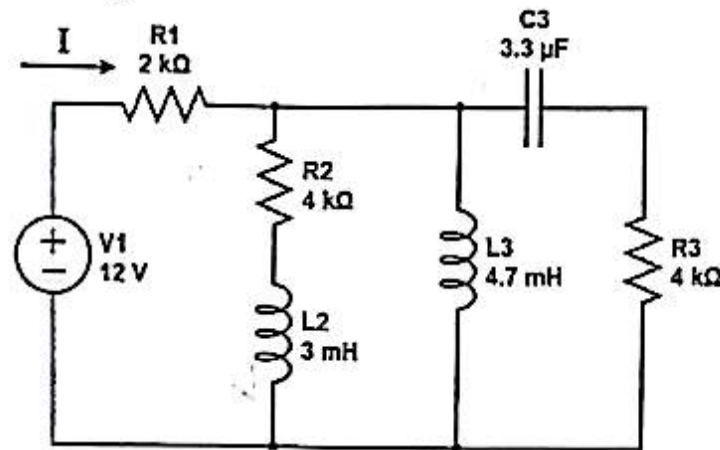

Q2. In a series RLC circuit, the source voltage is given by $v(t) = 20 \cos(\omega t)$, where $\omega = 10^3$ rad/s, the resistance $R = 400 \Omega$, the capacitance $C = 200 \mu\text{F}$. If the current flowing through the circuit is given by $i(t) = 35.58 \cos(\omega t - 44.64^\circ)$ mA, find the value of the inductance (L). (05)

Quiz – 01

Electrical Circuits II [0713-121]

Full Marks: 15


Time: 15 Minutes

ID:

Section:

Q1. Find the equivalent impedance of the following circuit.

(10)

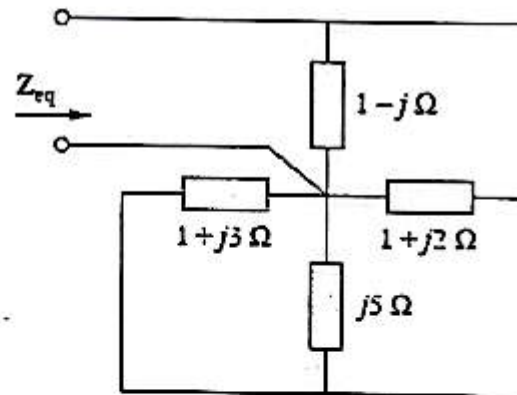

Q2. In a series circuit containing a $100\ \Omega$ resistor and an unknown capacitor, the voltage across the resistor and the capacitor are equal in magnitude. If the frequency is 60 Hz , calculate the capacitance C . (05)

Quiz – 01

Electrical Circuits II [0713-121]


Full Marks: 15

Time: 15 Minutes

ID:

Section:

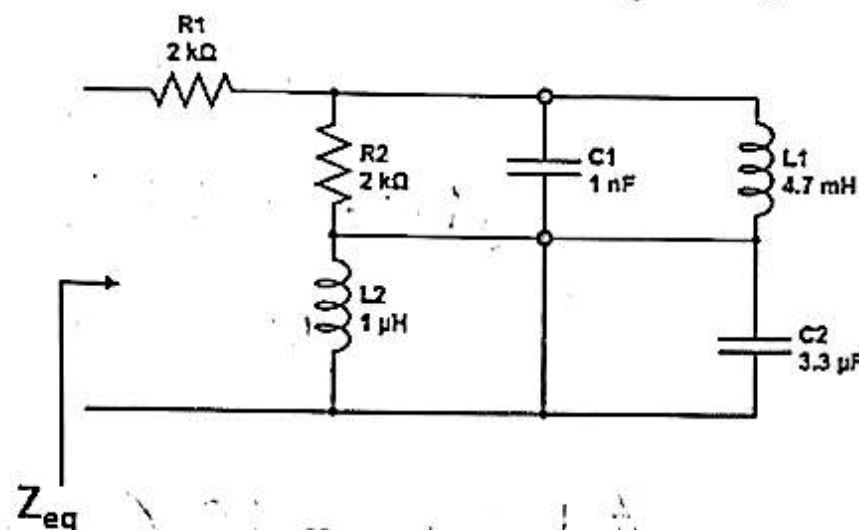- Q1. Determine the equivalent impedance of the following circuit, when $\omega = 10^3$ rad/s. (10)



- Q2. A branch has $Z_1 = 10 + j10\text{ }\Omega$. If you want to add a parallel capacitor X_c such that the total impedance is purely real, what must be the value of X_c ? (05)

Quiz - 03

Electrical Circuits II [0713-121]

Full Marks: 15

Time: 20 Minutes

ID:

Section:

- Q1. The circuit diagram in Fig. 1 represents a balanced 3-phase Y-Y system. Find the line current, and the average power delivered to the load. (07)
[Here, $Z_{Load} = 9 + j12 \Omega$, and $Z_{line} = 1 + j2 \Omega$]

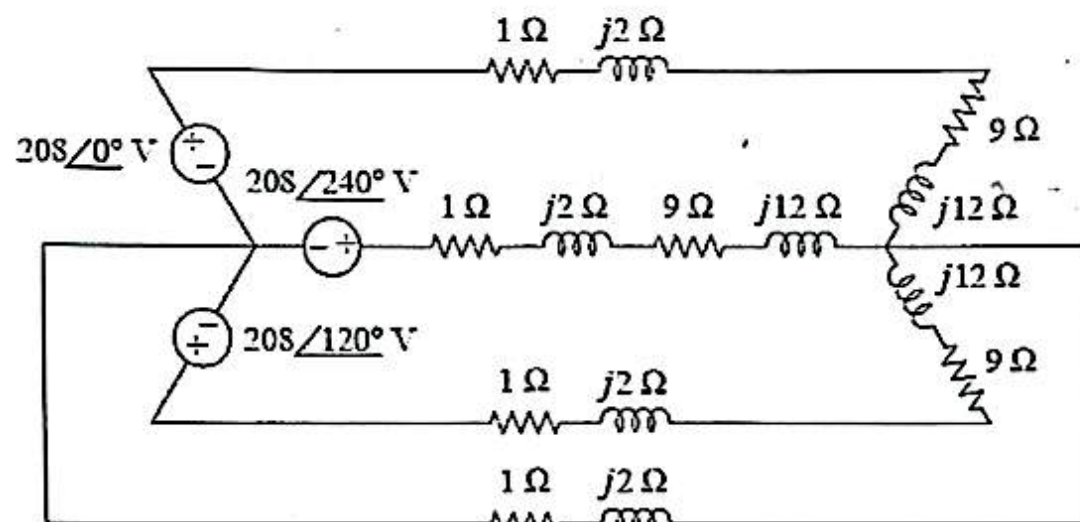


Fig. 1

- Q2. Two balanced loads are connected in parallel to a 13.8 kV (rms) line. Load 1 draws 500 kW at 0.7 lagging pf. Load 2 draws 300 kVAR at 0.9 lagging pf. Determine the total complex power and the overall power factor. (08)

Quiz – 04

Electrical Circuits II [0713-121]

Full Marks: 15

Time: 20 Minutes

ID:

Section:

Q1.

(08)

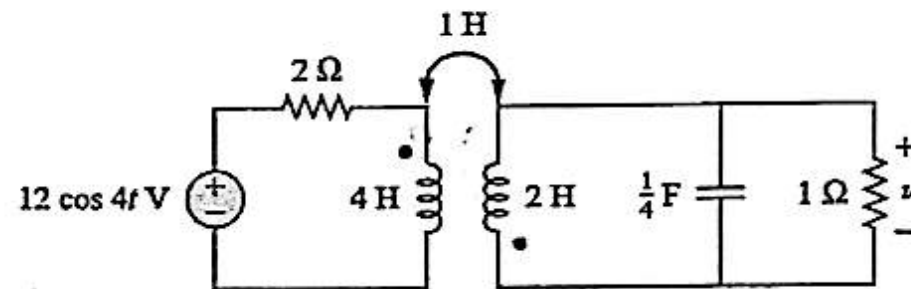


Fig. 1

- Find the coupling coefficient.
- Calculate v_o .
- Determine the energy stored in the coupled inductors at $t = 2 \text{ s}$.

- Q2. Design a bandstop filter that will reject a 200 Hz sinusoid while passing other frequencies. The required bandwidth is 100 Hz, and the only available resistor has a value of 150Ω . (07)

Quiz – 04

Electrical Circuits II [0713-121]

Full Marks: 15

Time: 20 Minutes

ID:

Section:

Q1.

(08)

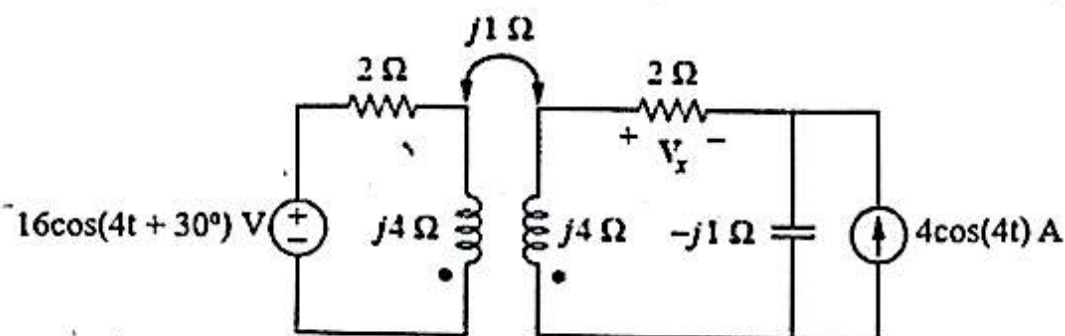


Fig. 1

- Find the coupling coefficient.
- Calculate V_x .
- Determine the energy stored in the coupled inductors at $t = 2 \text{ s}$.

- Q2. Design a bandpass filter with two half-power frequencies given by $\omega_1 = 20.1 \text{ kHz}$, and $\omega_2 = 20.3 \text{ kHz}$ respectively. The only available resistor has a value of $20 \text{ k}\Omega$. Determine the value of L , C . (07)