



**Daffodil International University**  
Department of Electrical and Electronic Engineering  
Faculty of Engineering  
**Mid-Term Examination, Summer'26**

Course Code: 0714-211  
Section: A, B, C, D, E, F, G  
Full Marks: 25

Course Title: Electronics I  
Level-Term: L2-T1  
Exam Date: July 01, 2026

Teacher's Initial: SD, KNA, KAH, MH  
Time: 1.5 Hours

[There are five (05) questions, answer all of them.]  
[The second right most column indicates the COs with respective Bloom's level.]  
[The right most column indicates the assigned marks.]

- Q1.** Suppose you need to construct a counter for counting products in a factory setup. Which type of Diode will you use for this case? Explain its working principle and how the diode is used for counting products with necessary diagrams. CO-1 [5]  
C(2)

Or

**Describe** the working principle of an n channel JFET with necessary diagrams. CO-1 [5]  
C(2)

- Q2.** Describe the operation of a Center-tapped Transformer Full Wave Rectifier with necessary diagrams. If the input to a Center-tapped Transformer [turns ratio 1:2] full wave rectifier made with Si diode is  $120\sin 60t$  V, determine (i) Average dc output voltage, (ii) PIV of the diodes. CO-2 [5]  
C(2)

- Q3.** Determine  $I_{D1}$ ,  $I_{D2}$ ,  $I_{D3}$  and  $V_O$  for the following circuit in Fig. Q3. CO-2 [5]  
C(3)

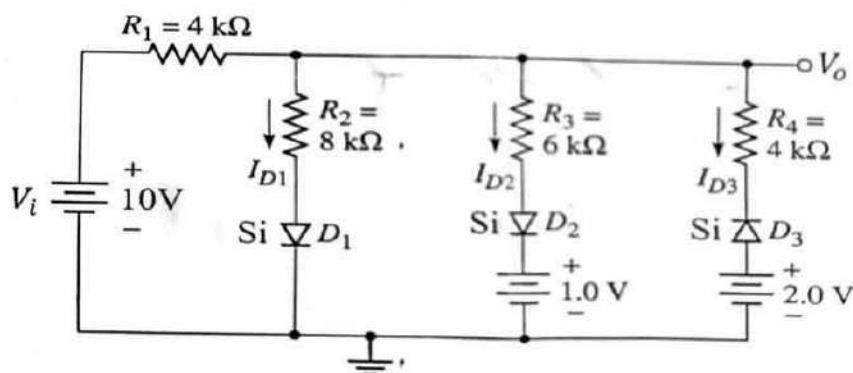


Fig. Q3

- Q4.** Determine and sketch the output signal of the following clipper circuit in Fig. Q4 for the given input signal. CO-2 [5]  
C(3)

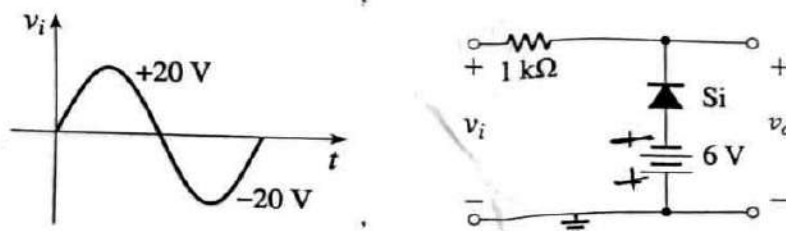


Fig. Q4

**Q5.**

For the following circuit in Fig. Q5, determine:

- (i) The minimum value of  $R_L$  to ensure that the Zener Diode is in the "on" state.
- (ii) The value of  $R_L$  that will establish maximum power conditions for the Zener diode.
- (iii) The range of  $I_L$  when  $V_L$  is being maintained at 24V.

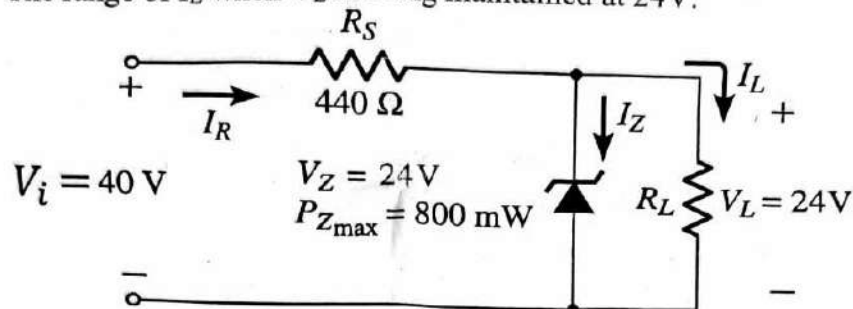
CO-2 [5]  
C(3)

Fig. Q5