



Daffodil International University
Faculty of Science & Information Technology (FSIT)
Department of Software Engineering
Midterm Examination, Summer 2025
Course Code: SE 213; Course Title: Digital Electronics and Logic Design


Sections & Teachers: SP, HI, MTE, NAN, SAN SHN
Batch and Section: 43 (A to O)

Time: 1 Hour 30 Mins

Marks: 25

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

 1.	a)	Subtract the following using 2's complement: i) $(17)_{10} - (63)_{10}$ ii) $(101100)_2 - (1011)_2$	[Marks-3+2]	CLO-1 Level-2
	b)	Check the following circuit diagram. Express the output logic equation and simplify it: 	[Marks-5]	
2.	a)	i) Construct the Full Adder circuit using basic logic gates. ii) Apply Parallel adder to compute $(X+Y)$ along with diagram: Where $X = 1011$ and $Y = 1100$	[Marks-5+2]	CLO-2 Level-3
	b)	$F(A, B, C, D) = (A+B)(C'+D) + A \cdot C$ Apply k-map simplification technique to simplify the above expressions. Construct the logic diagrams of the simplified output.	[Marks-8]	