



Daffodil International University
Department of Electrical and Electronic Engineering
Faculty of Engineering
Final Examination, Summer-2026

Course Code: 0714-323
Section: A, B, C, D, E
Full Marks: 40

Course Title: Digital Electronics
Level-Term: L3-T1
Exam Date: August 22, 2026

Teacher's Initial: DAS, BS
Time: 2 Hours

[Notes: Answer all the questions. The number on the rightmost side of the question indicates the marks]

- Q1. (a) Derive the truth table and, hence, draw the corresponding logic diagram for a BCD-to-decimal decoder. CO3 (C3) 6+5
(b) Implement the Boolean function, $F(A, B, C, D) = \sum(0, 1, 3, 5, 13)$ using a multiplexer. Use A, B, and D as the selection lines of the multiplexer.
- Q2. (a) Implement the following Boolean functions using PLA CO3 (C3) 5+3
 $F_1 = A'B'C' + A'BC + AB'C' + ABC$ and $F_2 = A'B'C + A'BC' + AB'C + ABC$
(b) JK flip flop is called the refinement of SR flip flop- Justify the statement with a suitable explanation. (C4)
- Q3. Consider a synchronous sequential circuit consisting of two JK flip-flops, A and B, with a single input x. The input equations of the flip-flops are given below: CO3 (C4) 10
 $J_A = x, K_A = B', J_B = x$ and $K_B = A$
(i) Draw the complete logic diagram of the sequential circuit.
(ii) Derive the state equations, construct the state table and draw the corresponding state diagram of the circuit.
- Q4. (a) Design a synchronous counter using T flip-flops that follows the counting sequence: CO3 (C3) 7+4
0, 1, 3, 4, 5, 7 and repeat.
(b) Draw and explain the operation of a 3-bit right-shift register using D flip-flops.

