

- Q3. (a) Design a counter with JK flip-flops which count binary sequence of 0, 1, 3, 2, 6, 4, 5, 7 and repeat. CO3 7+3
C3
- (b) Draw a 4-bit register using D flip-flops with parallel loading ability.
- Q4. The state diagram of a clocked sequential circuit is given in Figure 2. Design the circuit using T flip-flops and after detailed analysis draw the complete logic diagram of the circuit. CO3 10
C4

 


Figure 2



Daffodil International University
Department of Electrical and Electronic Engineering
Faculty of Engineering
Final Examination, Spring – 2026

Course Code: 0714-323

Course Title: Digital Electronics

Section: A, B, C

Level-Term: L3-T1

Teacher's Initial: DAS, BS

Full Marks: 40

Exam Date: April 25, 2026

Time: 2 Hours

[Notes: The number on the rightmost side of the question indicates the marks]

Answer all Questions

- Q1.** (a) Implement the following Boolean expressions using Decoder and external gates. CO3 6+4
C3
- $$F_1(x, y, z) = x'y'z' + xz$$
- $$F_2(x, y, z) = xy'z' + x'y$$
- $$F_3(x, y, z) = x'y'z + xy$$
- (b) An 8×1 multiplexer has inputs x, y , and z connected to the selection inputs s_2, s_1 , and s_0 respectively. The data inputs I_0 through I_7 are as follows: $I_1 = I_2 = I_7 = 0; I_3 = I_5 = 1; I_0 = I_4 = A; I_6 = A'$ C4
Determine the Boolean function implemented by the multiplexer.
- Q2.** (a) Design a combinational circuit using a PLA to convert BCD input into its corresponding Excess-3 code. CO3 6+4
C3
- (b) Write down the differences between combinational and sequential logic. A JK flip-flop is triggered by negative clock transitions. Draw the output waveform, Q for the flip-flop for the given clock and input waveforms as shown in Figure 1. Assume that the flip-flop is initially in the Reset state ($Q = 0$). CO3
C3

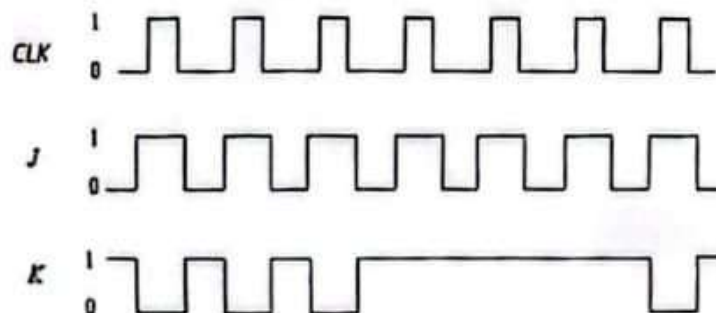


Figure 1